

الجامعة العربية الأمريكية  
ARAB AMERICAN UNIVERSITY



FACULTY OF ENGINEERING AND IT  
COMPUTER SYSTEMS ENGINEERING DEPARTMENT

## Digital Logic Design Lab Report

### Decoder and Encoder

Date: 17/12/2023

<b>Student Name:</b>	Ghayda' Ja'aysah
<b>Student ID:</b>	202110568
<b>Experiment Name:</b>	Decoder & Encoder
<b>Experiment No.:</b>	5
<b>Instructor Name:</b>	Asem Salah
<b>Supervisor Name:</b>	Eyas Al-souqi
<b>Section:</b>	2
<b>Partner Name if any:</b>	Saja Jaradat , Dareen AbuZaineh

## 1. OBJECTIVES

*This experiment aims to:*

- 1.to study the operating principle of decoder*
- 2. to implement applications of encoder .*
- 3. to study the operating principle of multiplexer*

## 2. INTRODUCTION

*We are in huge world of digital components*

*Today we will introduce to encoder and multiplexer .*

*We will study how does it work and how to implement several function using IC's in practical*

## 3. COMPONENTS REQUIRED:


ID	Component name	Amount
1	<u>Bread board , wires</u>	<i>1 , many</i>
2	<u>IC 74153 (4-1 multiplexer )</u>	<i>1</i>
3	<u>IC 74148 (8-to-3 Encoder)</u>	<u><i>1</i></u>

## 4. TASKS

- 1. Implement the function  $F(A,B,C)=\sum(0,1,4,7)$  USING 4-to-1 multiplexer*
- 2. Implement 8-to-3 Encoder*
- 3. Adding two BCD numbers using pre-implemented circuit in ETS-800*

## PART ONE : ENCODER

### 5. SYMBOLS AND DIAGRAMS

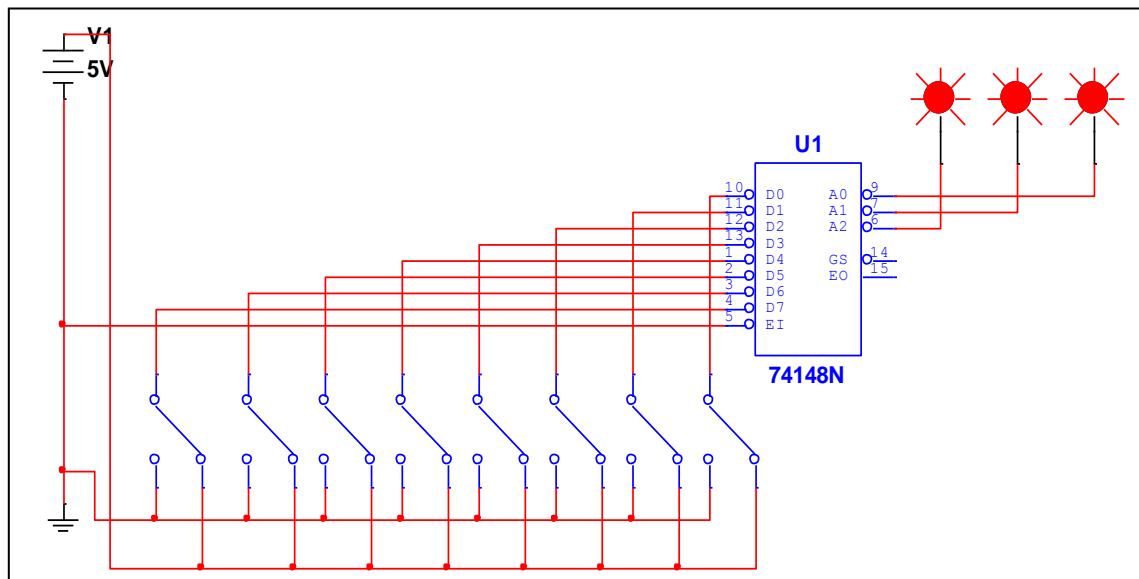

### 6. BOOLEAN EXPRESSION

$$A0 = D1' + D3' + D5' + D7'$$

$$A1 = D2' + D3' + D6' + D7'$$

$$A2 = D4' + D5' + D6' + D7'$$

### 7. TRUTH TABLE

Inputs									Outputs		
D7	D6	D5	D4	D3	D2	D1	D0	EI	A2	A1	A0
1	1	1	1	1	1	1	0	0	0	0	0
1	1	1	1	1	1	0	1	0	0	0	1
1	1	1	1	1	0	1	1	0	0	1	0
1	1	1	1	0	1	1	1	0	0	1	1
1	1	1	0	1	1	1	1	0	1	0	0
1	1	0	1	1	1	1	1	0	1	0	1
1	0	1	1	1	1	1	1	0	1	1	0
0	1	1	1	1	1	1	1	0	1	1	1

## 8. PROCEDURES

1. *Connect D0-D7 TO SW0-SW7 respectively*
2. *Connect A3 TO GND*
3. *Connect A2 , A1 , A0 directly to BCD displayer*
4. *Connect EO TO LED0*
5. *Connect GS to LED1*

## 9. EXPERIMENT RESULTS

Inputs									Outputs		
D7 SW7	D6 SW6	D5 SW5	D4 SW4	D3 SW3	D2 SW2	D1 SW1	D0 SW0	EI GND	A2 C	A1 B	A0 A
0	0	0	0	0	0	0	0	0	GREEN	GREEN	GREEN
5V	5V	5V	5V	5V	5V	5V	5V	0	RED	RED	RED
0	5V	5V	5V	5V	5V	5V	5V	0	GREEN	GREEN	GREEN
5V	0	5V	5V	5V	5V	5V	5V	0	GREEN	GREEN	RED
5V	5V	0	5V	5V	5V	5V	5V	0	GREEN	RED	GREEN
5V	5V	5V	0	5V	5V	5V	5V	0	GREEN	RED	RED
5V	5V	5V	5V	0	5V	5V	5V	0	RED	GREEN	GREEN
5V	5V	5V	5V	5V	0	5V	5V	0	RED	GREEN	RED
5V	5V	5V	5V	5V	5V	0	5V	0	RED	RED	GREEN
5V	5V	5V	5V	5V	5V	5V	0	0	RED	RED	RED

## 10. DISCUSSIONS AND CONCLUSIONS

*Our decoder inputs work on low voltage . that mean all inputs should be active unless the input you want to select(disply ) it should was in-active , but we come with small problem (significant digits)*

*We connect D7 with SW7 which the most significant digit . but unfortunately the job woks the other way around .*

*D0 active 1 1 1 which indicate to D7 , we can solve this problem by swapping the wires .*

*Another thing we came into , that this circuit is low priority , which mean if D0 and D3 zero's*

*The output will be 000 not 011 .*


*So if you want to work as significant digits you have to swap wires which means*

*D0 WITH most-significant digit*

*D7 WITH least-significant digit .*

## PART 2 : implement $F=(0,1,4,7)$ USING 4-1 Multiplexer

### 11. SYMBOLS AND DIAGRAMS

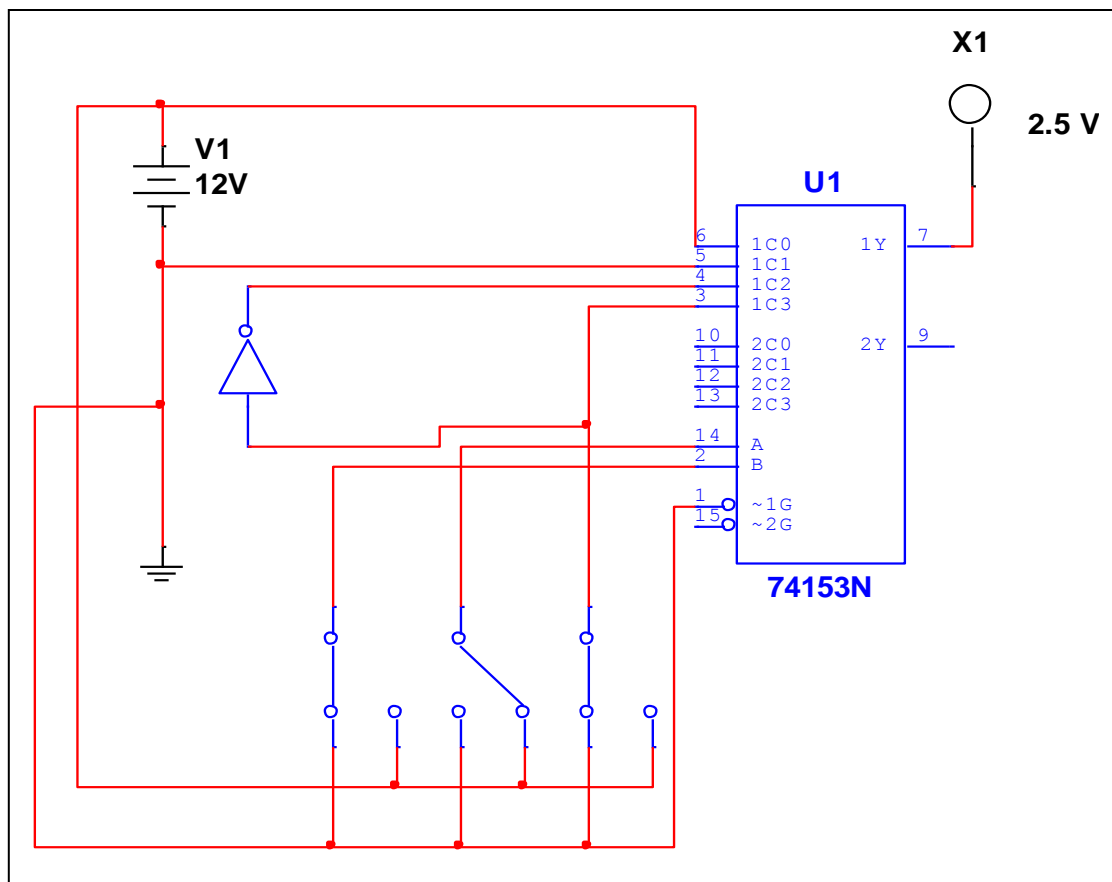

### 12. BOOLEAN EXPRESSION

$$I_0 = 1$$

$$I_1 = 0$$

$$I_2 = C'$$

$$I_3 = C$$

### 13. TRUTH TABLE

Input			Output
A	B	C	F
0	0	0	1
0	0	1	1
0	1	0	0
0	1	1	0
1	0	0	1
1	0	1	0
1	1	0	0
1	1	1	1

## 14. PROCEDURES

1. Connect I0 to VCC
2. Connect I1 to GND
3. Connect I2 to C'
4. Connect I3 to C
5. Connect C to SW1
6. Connect B to SW2
7. Connect A to SW3
8. Connect F to LED6

## 15. EXPERIMENT RESULTS

Input			Output
A SW3	B SW2	C SW1	F LED6
0	0	0	RED
0	0	5V	RED
0	5V	0	GREEN
0	5V	5V	GREEN
5V	0	0	RED
5V	0	5V	GREEN
5V	5V	0	GREEN
5V	5V	5V	RED

## 16. DISCUSSIONS AND CONCLUSIONS

*The multiplexer have four inputs , one output , in this experiment we have to implement the function above using multiplexer so we have to decide the relation between input to have the correct output .*

*We have 3 inputs A , B , C we decide to let A,B the selector .*

*And Compare F with C for same value of A,B .*

*Our experiment done successfully and we come into the correct output .*

*The multiplexer decide the output according to it's inputs*